

UNIVERSITY OF TÜBINGEN

Solar cell

BLOCKPRAKTIKUM 2021

First Version

Christian Gommeringer Matthias Gatter Jonathan Witte
Eduard Heidt David Schütz

overlooked by Tao Wei

March 16, 2022

Contents

1	Introduction	3
2	Theoretical Fundamentals	3
2.1	Questions	3
2.2	p-n-Transition of a diode	5
2.3	Internal photoelectric effect	6
2.4	Photovoltaic effect	6
2.5	One-Diode-Model	7
2.6	Cell parameters	8
2.6.1	Short circuit current	9
2.6.2	No-load voltage	9
2.6.3	Maximum Power Point	9
2.6.4	Fill factor	9
2.6.5	Energy conversion efficiency	9
2.6.6	Parallel resistance	9
2.6.7	Serial resistance	9
3	Execution of the experiment	10
4	Evaluation of the measured data	10
5	Conclusion	22

1 Introduction

A solar cell converts photonenergy into a electrical energy which is usable in form of a electric current. In this experiment we analyse the behavior of a solar cell in different views of physical description. First we talk about the theoretical fundamentals to make us clear about the physical relations. After that we describe the experiment and it's execution. All in all we then hand over to the analysis of our measurements and present our results.

2 Theoretical Fundamentals

2.1 Questions

What is the difference between metals, insulators and semiconductors?

Answer: An insulator has in band theory a unoccupied conduction band cause of the big band gap. So in low and high temperatures are only a few electrons which are thermally stimulated from the valence band into the conduction band. Semiconductors have a much smaller band gap, which makes it possible for electrons by thermal stimulation to get up to the conduction band. The band gap is moveable. A semiconductor has a low conductivity in room temperature and the conductivity can be increased by heating the semi conductor. In metals the band gap is very small or the valence band and the conduction band are overlapping. This makes a metal a good conductor by room temperature.

What is the role of electrons, holes, and doping in semiconductor's physics?

Answer: If a elektron is thermally stimulated in the valence band, it jumps over the the conduction band. So there is now a hole in the valence band which can be filled, for example a atom and at this point we have doting. There are two types of doting, n-doting where you bring in an atom which one of the electrons is weak bounded an can easily stimulated into the conduction band, such atoms are called electron donators and on the other side we have p-doting, where the atom has an electron missing and can take electrons from the conduction band in their boundness and bring them into the valence band, such atoms are called electron acceptors.

How is a semiconducting diode build up? What is the diode equation and how does the IV curve of a diode looks like?

Answer: The base of a semiconducting diode is a p-n-doted semiconducting crystal or a metal-semiconductor-transition (Schottky Diode). The conductivity of such a transition depends on the polarity of the operating voltage on the anode (p-doted) and cathode (n-doted), also it depends on the current direction. The p-n-transition (grey zone) is a

zone where charges can move freely, cause positive charges (defect electrons or holes) of the p-doped crystal and negative charges (free electrons) of the n-doped crystal are diffusing on the other side of the p-n-transition and are disappearing cause of recombination. The origin of the charges are doped atoms which are fixed in position and they are forming as ions a space charge, which electrostatic field is building space charge zone which keeps the two sides separated and stops more recombination. Over the whole space charge zone is forming a diffusing voltage. The diffusing voltage can through an outside applied voltage be compensated, then the p-n-transition can be conductive or be strengthened, then it keeps blocked.

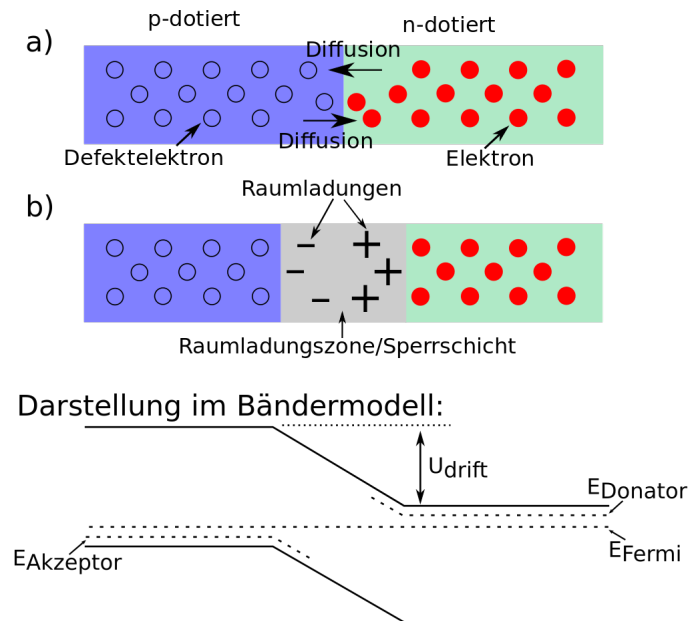


Illustration 1: p-n-transition, source: <https://de.wikipedia.org/wiki/Diode#/media/Datei:Sperrschicht.svg>

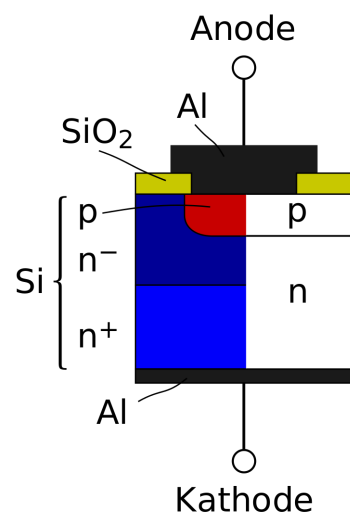


Illustration 2: Schematic example of a p-n-diode: source: <https://de.wikipedia.org/wiki/Diode#/media/Datei:Pn-Diode-Aufbau.svg>

The diode equation is given by

$$I_D = I_S(T) \left(\exp \left(\frac{U_F}{nU_T} - 1 \right) \right) \quad (1)$$

where I_D is the diode current, $I_S(T)$ the temperature dependent saturation current, U_F the forward voltage, n the emission coefficient, $U_T = \frac{k_B T}{e}$ the temperature voltage, k_B the boltzmann constant, e the elementary charge. We also take a look at the characteristic curve of a diode current.

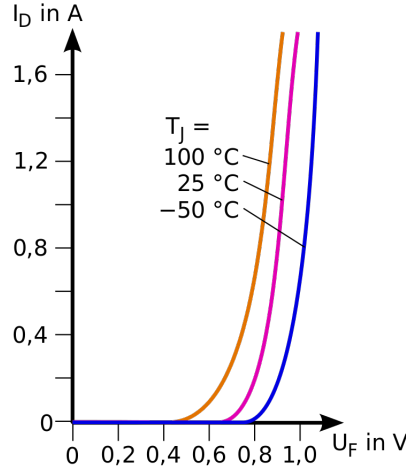


Illustration 3: Characteristic curve of the diode, source: https://de.wikipedia.org/wiki/Shockley-Gleichung#/media/Datei:Dioden-Kennlinie_1N4001.svg

What ist the internal photoelectric effect and what is the photovoltaic effect?

How does the IV-curve of a solar cell looks like? How can the most important cell parameters be extracted from the IV curve, i.e., the short circuit current, the open circuit voltage, the maximum power point, the fill factor, the efficiency, the parallel resistance and the serial resistance?

These two Questions will be later discussed and answered.

2.2 p-n-Transition of a diode

Many solar types are made of the semiconductor material silicon. A crystal silicon solar cell is made of p-doted silicon-layer (base) which is in contact with a n-doted silicon-layer (emitter). In the contact zone between this two layers is forming the p-n-transition, which determines the physics of the solar cell. Cause of the concentration gradient of the charges in the contact zone, the holes are diffusing out of the p-zone into the n-zone and conversely electrons from the n-zone into the p-zone. In the p-zone are staying negative ionised acceptors and in the n-zone are staying positive ionised donators as fixed space charge. The space charge with diffent polarity on both sides of the interface leads to a

electric field, that's forming a field current against the direction of the diffusing current which leads to a compensation.

2.3 Internal photoelectric effect

If light shines on a solar cell, photons with energy greater or equal the band gap of the semiconductor material are getting absorbed. A absorbed photon leads to that a bound electron in the valence band is getting thermally stimulated and jumps to a niveau of the conduction band of the semiconductor. Together with to hole in the valence band they form a moveable electron-hole-pair.

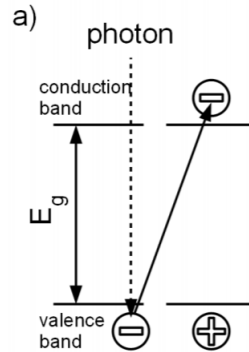


Illustration 4a: Schematics of the internal photoelectric effect. Source: experiment instruction

2.4 Photovoltaic effect

Gets a photon in the space charge zone absorbed of the solar cell, it equalizes the electric field around the electron-hole-pair. The electron moves into n-zone und the hole into the direction of the p-zone. Gets the electron-hole-pair formed beyond the space charge region, so it cans by thermal motion diffuse into the space charge region. The electrons in the p-zone an the holes in the n-zone are getting accelerated onto the opposing side by the electric field of the space charge zone. Together the charges whiche are formed in the contact region , they form the photo current I_{ph} . Electrons in the p-zone are moving to the n-zone and the holes are moving from the n-zone to the p-zone. The p-side now gets positively charged and the n-side negatively, the potential difference can be tapped as no-load voltage. This process of light induced charge segregation at the p-n-transition of the diode is called photovoltaic effect.

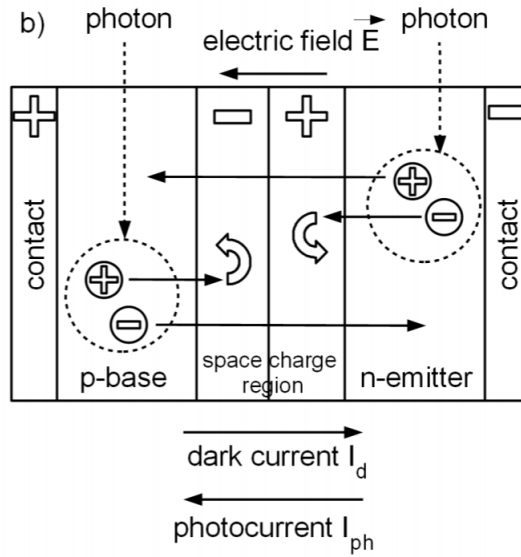


Illustration 4b: Schematics of the photovoltaic effect. Source: experiment instruction

2.5 One-Diode-Model

In the following we derive the characteristic I-V-line of the solar cell. Every contribution of the output current I can be illustrated by a equivalent circuit diagram of a real solar cell.

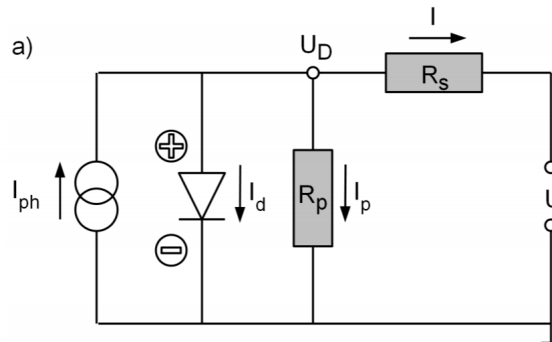


Illustration 5a: equivalent circuit diagram, source: experiment instruction

The solar cell let itself be understood as parallel circuit of a current source, a forward poled diode, and of a parallel resistance R_p . The drawn current source delivers the constant photo current I_{ph} . The photo current I_{ph} gets reduced through the diode current I_d , through the current I_p and through the parallel resistance R_p . The serial resistance reduces the output current and the tapped voltage. A unlit solar cell behaves like a diode cause of the p-n-transition. For a ideal diode is the IV-curve given by the diode equation

$$I_d(U_D) = I_0 \left[\exp \left(\frac{eU_D}{nk_B T} \right) - 1 \right] \quad (2)$$

where I_d is the dark current, I_0 the saturation current, U_D the voltage drop over the diode, T the cell temperature. The diode factor n is approximately one. $n \approx 1$. The saturation current I_0 gets calculated by the diffusion coefficients, the diffusion lengths for electrons and holes, the donor- and activator concentration and the intrinsic charge carrier density leads to a temperature dependence

$$I_0(T) \propto T^s \exp\left(-\frac{E_g}{k_B T}\right) \quad (3)$$

where E_g is the band gap energy and s a material dependent exponent ($s = 0$ for silicon). The IV-curve of an ideal solar cell is then given through

$$I_D(U_D) = I_{ph} - I_d(U_D) \quad (4)$$

$$I_D(U_D) = I_{ph} - I_0 \left[\exp\left(\frac{eU_D}{nk_B T}\right) - 1 \right] \quad (5)$$

Photo current and dark current are running in opposing directions, where the dark current runs from p-zone to n-zone, like a forward poled diode. For a real solar cell we have to consider the parallel resistance R_p and the serial resistance R_s . With $R_p = U_D/I_p$ and $R_s = (U_D - U)/I$ it follows

$$I(U_D) = I_{ph} - I_d(U_D) - I_p(U_D) \quad (6)$$

$$I(U) = I_{ph} - I_0 \left[\exp\left(\frac{e(U + IR_s)}{nk_B T}\right) - 1 \right] - \frac{U + IR_s}{R_p} \quad (7)$$

with output current I and output voltage U , which can be tapped at the solar cell.

2.6 Cell parameters

Out of the IV-curves it is possible to calculate the cell parameters approximately.

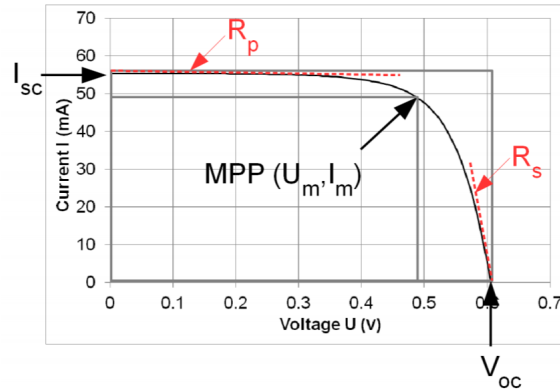


Illustration 6: Determination of cell parameters, source: experiment instruction

The parameters can be extracted of certain characteristics of the the I-U curves, often in approximated way. We want to use these equations later on in order to evaluate our data further.

2.6.1 Short circuit current

$$U = 0V$$

$$I_{sc} \approx I_{ph} \left(1 + \frac{R_s}{R_p} \right) \quad (8)$$

2.6.2 No-load voltage

$$I = 0A$$

$$V_{oc} \approx \frac{k_B T}{e} \ln \left(\frac{I_{sc}}{I_0} \right) \quad (9)$$

2.6.3 Maximum Power Point

Describes the point (U_m, I_m) of a IV-curve with the most useable output power.

$$P_{MPP} = U_m \cdot I_m = P_{out, \max} \quad (10)$$

2.6.4 Fill factor

$$FF = \frac{U_m I_m}{I_{sc} V_{oc}} = \frac{P_{MPP}}{I_{sc} V_{oc}} \quad (11)$$

2.6.5 Energy conversion efficiency

Irradiated power P_{in} . Irradiated area A . Irradiance E_e .

$$\nu = \frac{P_{MPP}}{P_{in}} = \frac{P_{MPP}}{AE_e} \quad (12)$$

2.6.6 Parallel resistance

Slope in point $(U = 0V, I = I_{sc})$ is approximately the parallel resistance.

$$R_p \approx \left[- \left(\frac{\partial I}{\partial U} \right)_{I_{sc}} \right]^{-1} \quad (13)$$

2.6.7 Serial resistance

Slope in point $(U = V_{oc}, I = 0A)$ is approximatley the serial resistance.

$$R_s \approx \left[- \left(\frac{\partial I}{\partial U} \right)_{V_{oc}} \right]^{-1} \quad (14)$$

3 Execution of the experiment

By measuring the U-I curve of a irradiated solar cell we want to determine several of it's characteristic parameters. In our experiment we used a halogen lamp with following properties 12 V, 35 W, output angle 10° , color temperature 3000 K, maximum luminosity intensity 11000 Cd. We installed this lamp and the solar cell on a rail, on which their position was variable. We adjusted the vertical position of the solar cell until it was lightened in an optimal way. After that we gave the lamp some time to reach it's full irradiation power. In the mean time we changed the distance between cell and lamp in order to get some intuition for which effect these changes have on the short circuit current of the solar cell. We decreased the illumination intensity by decreasing the lamp current. As a consequence the short cut current decreased from 67 mA original value to 44.5 mA. This shows an non linear reaction of the solar cell to the illumination power. The second thing, we examined, was the effect of doubling of the distance between lamp and cell. That decreased the short cut current to 26.8 mA. We also measured the new obtained intensity on the surface of the cell in this setting. This showed an decrease to 42% of the original illumination intensity. For a homogeneous radiation of the lamp we would of course expect only one fourth of the original intensity. This can only be explained by a inhomogeneous radiation of the lamp, that concentrates it's power in the center of one irradiation direction.

After the the acquired time passed for the lamp to reach it's thermal equilibrium we set up the cell on a position, where the short circuit current was 60 mA and then we measured the I-U curves for four different cases.

First we measured with no additional load than the 10-turn-potentiometer, then we applied a resistance parallel to the potentiometer and our measuring equipment. The third time we applied a resistance in series. And for the last time we reduced the short circuit current to 30 mA and repeated the first measurement without load.

For the recording of the I-U curves we proceeded the same way for all four cases. We increased the resistance in 1Ω steps from zero to 30Ω and then in 5Ω steps from 30Ω to 60Ω , and after that in 10Ω steps until 120Ω .

4 Evaluation of the measured data

We executed the experiment as described and obtained the data which is presented on the following two pages. Out of that data we can draw the I-U curves of the solar cell for each case and compare them with each other.

I_1 in mA	U_1 in mV	I_1 in mA	U_1 in mV
0.26	60.1	0.203	48.5
0.31	57.2	0.24	45.1
0.34	54.6	0.263	42.7
0.37	50.9	0.285	40.2
0.39	47.8	0.304	37.8
0.41	45.2	0.318	35.8
0.43	41.8	0.333	33.7
0.44	38.8	0.348	31.2
0.45	36.4	0.357	29.8
0.459	34.3	0.366	28
0.465	32.3	0.374	26.6
0.469	30.8	0.378	25.7
0.473	29.3	0.385	24.3
0.477	27.7	0.39	23.2
0.481	26.3	0.395	22.2
0.484	25	0.399	21.2
0.486	23.9	0.403	20.1
0.488	23.1	0.406	19.5
0.49	22	0.409	18.8
0.493	21	0.412	18
0.494	20.4	0.415	17.2
0.495	19.6	0.417	16.7
0.497	18.8	0.419	16
0.498	18.2	0.421	15.5
0.499	17.5	0.423	15.1
0.5	17.1	0.424	14.6
0.501	16.5	0.426	14.2
0.502	15.9	0.427	13.8
0.503	15.4	0.428	13.4
0.504	15	0.43	12.9
0.504	14.6	0.431	12.6
0.508	12.8	0.436	11
0.51	11.4	0.439	9.9
0.512	10.3	0.442	8.9
0.513	9.4	0.444	8.2
0.515	8.6	0.446	7.5
0.516	8	0.448	6.9
0.518	6.9	0.45	6
0.519	6.1	0.452	5.3
0.52	5.03	0.454	4.8
0.521	4.59	0.455	4.3
0.521	4.22	0.456	3.9
0.522	3.92	0.456	3.6

Table 1: measurement data for the 1. and 2. case

I_3 in mA	U_3 in mV	I_4 in mA	U_4 in mV
0.179	44.7	0.117	29.4
0.212	41.3	0.146	29.2
0.236	38.7	0.149	29.2
0.257	36.3	0.177	29
0.272	34.5	0.212	28.5
0.288	32.6	0.235	28.1
0.303	30.8	0.268	27.3
0.318	29	0.292	26.6
0.331	27.3	0.306	26
0.34	26	0.322	25.2
0.351	24.7	0.336	24.5
0.357	23.9	0.349	23.7
0.365	22.9	0.359	22.9
0.371	22	0.371	22
0.378	21.1	0.381	21.2
0.385	20.1	0.388	20.6
0.389	19.5	0.395	19.8
0.395	18.8	0.401	19.5
0.399	18.1	0.406	18.6
0.404	17.5	0.412	17.9
0.408	16.9	0.416	17.4
0.412	16.4	0.42	16.8
0.415	15.9	0.424	16.3
0.419	15.4	0.427	15.8
0.422	15	0.43	15.3
0.425	14.6	0.433	14.9
0.428	14.1	0.436	14.5
0.43	13.7	0.437	14.3
0.433	13.4	0.44	13.7
0.435	13.1	0.443	13.3
0.438	12.7	0.445	13
0.447	11.3	0.453	11.4
0.455	10.3	0.459	10.3
0.462	9.3	0.463	9.4
0.467	8.6	0.467	8.6
0.471	8	0.47	7.9
0.475	7.3	0.472	7.3
0.482	6.4	0.476	6.4
0.486	5.7	0.479	5.6
0.49	5.2	0.481	5
0.494	4.7	0.483	4.6
0.496	4.3	0.484	4.2
0.499	4	0.486	3.9

Table 2: measurement data for the 3. and 4. case

Out of these results the following I-U curves arise.

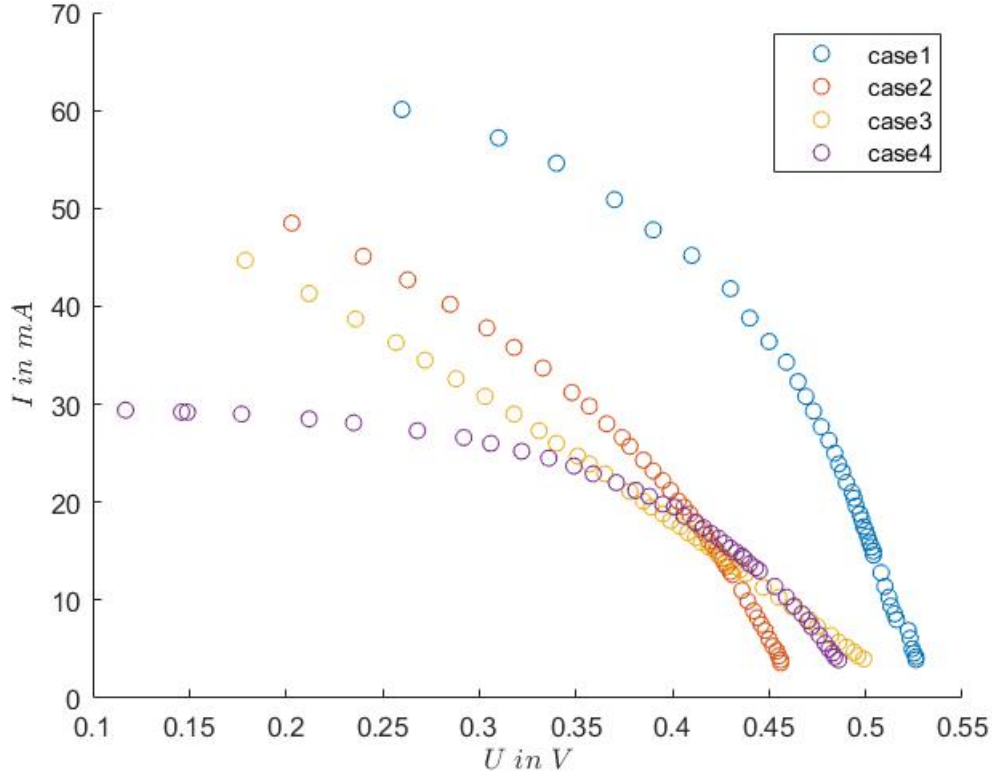


Figure 1: the I-U curve for all 4 different measurements

Out of these diagram and the measured data it becomes noticeable that we lack of parts of the curve, which are needed to determine all parameters. Therefore we have to fit those curves in order to get access to the missing curve parts. From the theory we know that the course of $I(U)$ follows the relation

$$I(U) = I_{ph} - I_0 \left(\exp \left(e \frac{U + R_s I}{n k_B T} \right) - 1 \right) - \frac{U + R_s I}{R_p}$$

This is an equation, that first has to solved for I. Doing this I take advantage of the lambert w function, for which holds

$$z = x e^x, \quad \text{only if } x = w(z)$$

The starting equation can be reshaped as follows

$$\left(1 + \frac{R_s}{R_p} \right) I = I_{ph} + I_0 - \frac{U}{R_p} - I_0 \exp \left(e \frac{U + R_s I}{n k_B T} \right)$$

In general it holds for

$$\begin{aligned}
x &= a - b \cdot e^{cx} \\
(x - a) e^{-cx} &= -b \\
-c \cdot (x - a) e^{-c(x-a)} &= cb e^{ca} \\
\Rightarrow -c(x - a) &= w(cb e^{ca}) \\
x &= a - \frac{1}{c} w(cb e^{ca})
\end{aligned}$$

When we transfer this result to our particular case, I can be written as

$$\begin{aligned}
I(U) &= \frac{I_{ph} + I_0}{1 + \frac{R_s}{R_p}} - \frac{U}{R_p + R_s} \\
&\quad - \frac{nk_B T}{e R_s} w \left(\frac{I_0}{1 + \frac{R_s}{R_p}} \frac{e R_s}{nk_B T} \exp \left(\frac{e U}{nk_B T} \right) \cdot \exp \left(\frac{e R_s}{nk_B T} \cdot \left(\frac{I_{ph} + I_0}{1 + \frac{R_s}{R_p}} - \frac{U}{R_p + R_s} \right) \right) \right)
\end{aligned}$$

where R_s is the internal resistance in series R_p is the internal parallel resistance and n is a dimensionless factor. If we consider the cases 2 and 3, where additional resistance is applied, the equation doesn't change fundamentally. It only holds that the resistances transit to

$$R_s \rightarrow R_{s,0} + R'_s$$

if an additional resistance in series is applied. And

$$R_p \rightarrow R_{p,0} + R'_p$$

Therefore the form of the expression for the current stays the same.

I approximated all 4 curves with a function of the form

$$I = a_1 + a_2 - a_3 U - \frac{1}{a_4} w [a_4 a_2 \exp(a_5 U) \exp(a_4 \cdot (a_1 + a_2 - a_3 U))]$$

and obtained following results.

The curve 1 could be approximated using the parameters

$$a_1 = 81.6695 \quad a_2 = 1.8 \cdot 10^{-7} \quad a_3 = 80.7537 \quad a_4 = 0.0399 \quad a_5 = 35.9712$$

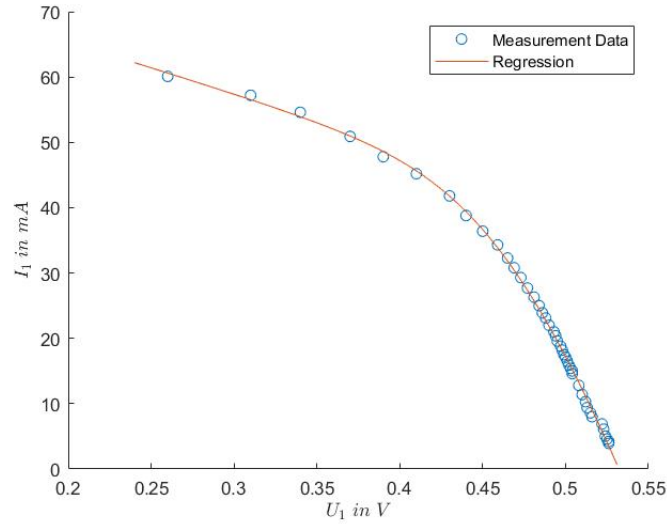


Figure 2: the course of the measured points of the first I-U curve with a regression

for the 2. measurement I obtained

$$a_1 = 63.933 \quad a_2 = 0.246 \quad a_3 = 66.525 \quad a_4 = 1.7 \cdot 10^{-5} \quad a_5 = 10.528$$

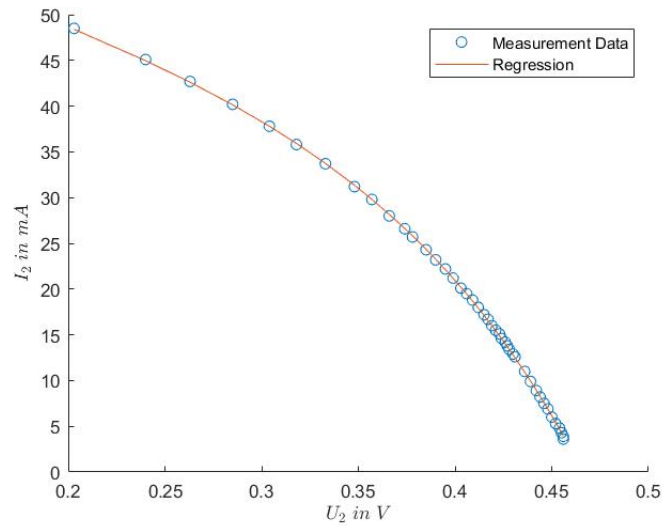


Figure 3: the course of the measured points of the 2. I-U curve with a regression

for the 3. case the following parameters were found

$$a_1 = 137.136 \quad a_2 = 46.036 \quad a_3 = 2.7 \cdot 10^{-4} \quad a_4 = 0.014 \quad a_5 = 2.595$$

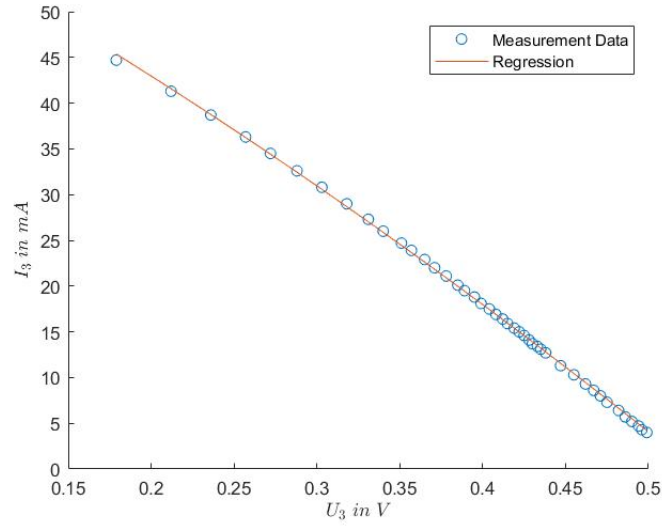


Figure 4: the course of the measured points of the 3. I-U curve with a regression

and finally for the 4. data set these results were found

$$a_1 = 29.93 \quad a_2 = 0.172 \quad a_3 = 0.035 \quad a_4 = 8.3 \cdot 10^{-6} \quad a_5 = 10.354$$

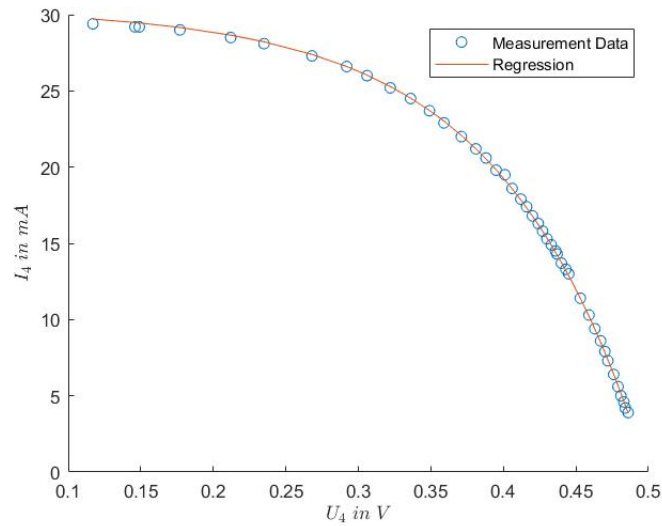


Figure 5: the course of the measured points of the 4. I-U curve with a regression

Using the relation $P = I \cdot U$ we can depict the course of the power in dependence of the voltage.



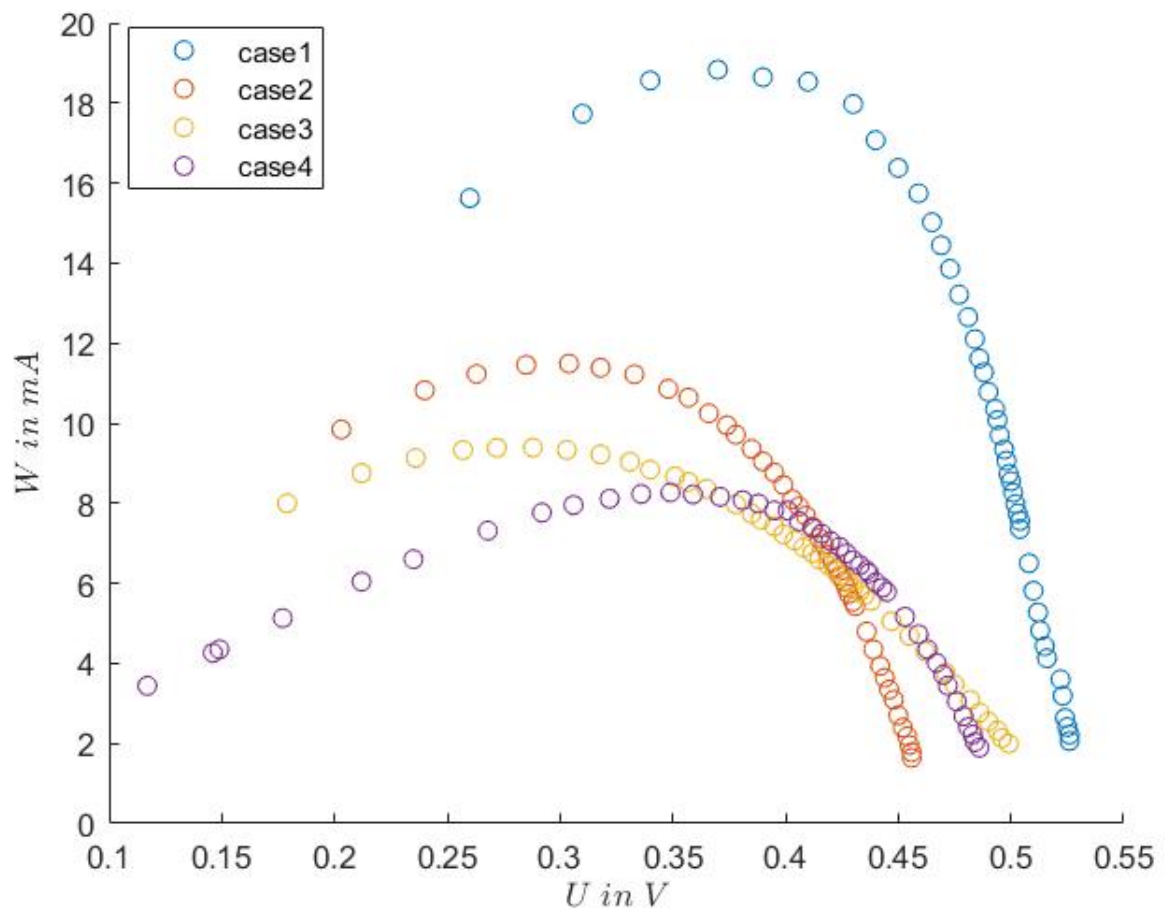


Figure 6: the course of the power for all four different measurements

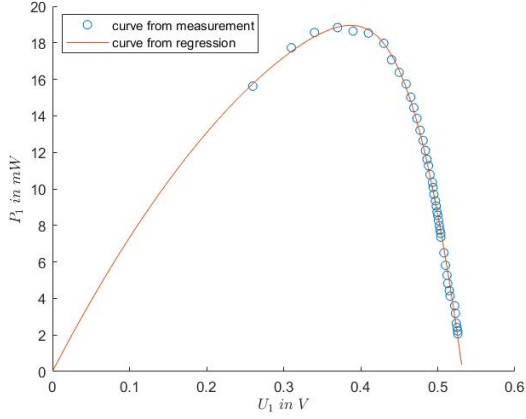
In the following the power curves along with the curves obtained the fit functions from above are shown.




(a) power curve 1

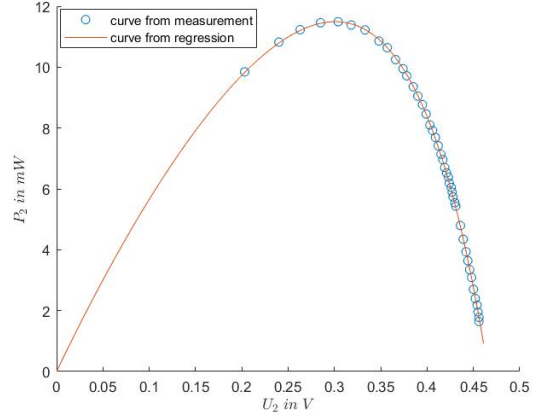

(b) power curve 2

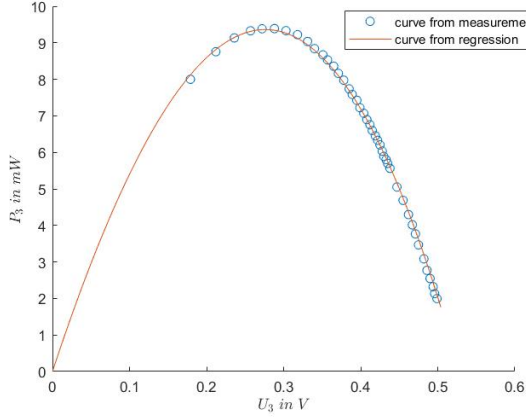

(c) power curve 3

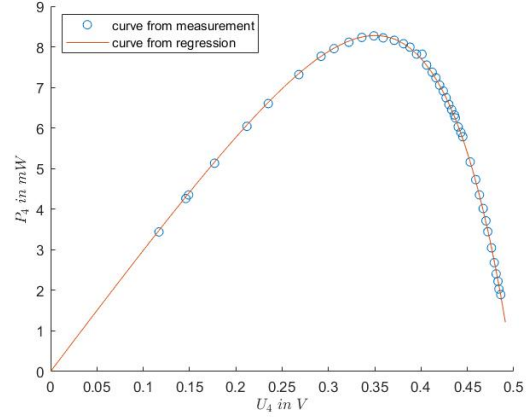

(d) power curve 4

Figure 7: the the power curves of the different measurement with the power curves using the parameters of the previous fits

Using the regression functions, I calculated the characteristics of the different settings of each case, which are collected in the following table. We measured the irradiated area of the solar cell to 78 mm^2 and the illumination intensity to $E_v = 27000 \text{ lux}$ for the first three measurements and $E_v = 102500 \text{ lux}$ for the fourth measurement. This values where were converted into irradiance intensity E_e by using the special luminous efficacy $K = E_v/E_e \approx 300 \text{ lm/W}$. For the calculation of I_{sc} and U_{oc} I used the relations $I_{sc} = I(U = 0)$ and $V_{oc} = U(I = 0)$.

case	measurement	E_e (W/m ²)	I_{sc} (mA)	V_{oc} (V)	P_{MPP} (mW)	FF (%)	η (%)	R_p (Ω)	R_s (Ω)
1	$I_{sc} = 60 \text{ mA}$	900	81.669	0.532	18.943	43.579	26.985	12.383	1.728
2	$I_{sc} = 60 \text{ mA}$ $R_p = 15 \Omega$	900	63.932	0.466	11.526	38.709	16.419	14.467	2.405
3	$I_{sc} = 60 \text{ mA}$ $R_s = 5.1 \Omega$	900	67.802	0.532	9.37	25.971	13.348	8.561	7.325
4	$I_{sc} = 30 \text{ mA}$	341.667	29.93	0.499	8.282	55.442	31.076	552.323	3.211

Table 3: the results of the evaluation using the fit parameters

We can observe that the short cut current and the open circle voltage are less influenced by the additional connection of the parallel resistance than of the serial resistance, but the efficiency drops more when the serial resistance is linked up than for the parallel pendant. We can now test our fit solution on how consistent it relates the resistances. It should hold

$$R_{p,2} \stackrel{!}{=} R'_{p,2} := \left(\frac{1}{R_{p,1}} + \frac{1}{15 \Omega} \right)^{-1}$$

But the result for $R'_{p,2} = 6.783 \Omega$, whereas $R_{p,2} = 14.467 \Omega$. This is quite far away from the reality. For the serial resistance the results are better.

The difference $\Delta R_s := R_{s,3} - R_{s,1} = 5.597 \Omega$, while it should be the 5.1Ω from the additional serial resistance. The situation that, the approximation for R_s seems to be far better than for R_p , can probably be explained by considering, that the measured data points are way closer to the x-axis cross section than to the y-axis cross section. Therefore the regression should be better in this part of the I-U curve. This might explain, too, why the resistance $R_{p,4}$ with 552Ω seems to be completely out of range, whereas it should be the same as for case 1.

The values for the efficiency can be assessed as quite good, because the values could have been taken from the measured data directly, and therefore have been calculated from a part of the regression which fitted very well to the data.

In the end I want to examine the effect of the temperature on the I-U curve and the characteristics of the solar cell. I proceed that by running a matlab simulation, which was provided to us by the university. With a chosen short cut current of 60 mA I examine the effect of the temperature by evaluating the I-U curves for the 25°C, -15°C and 40°C.

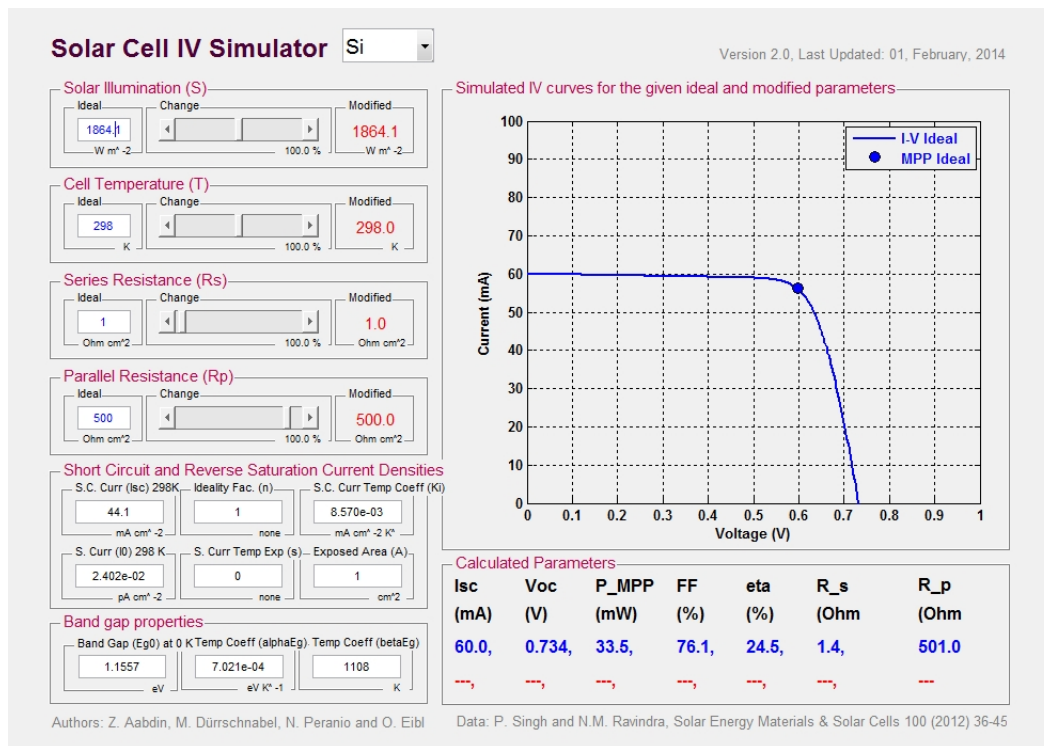


Figure 8: The simulation of the I-U curve for 25°C

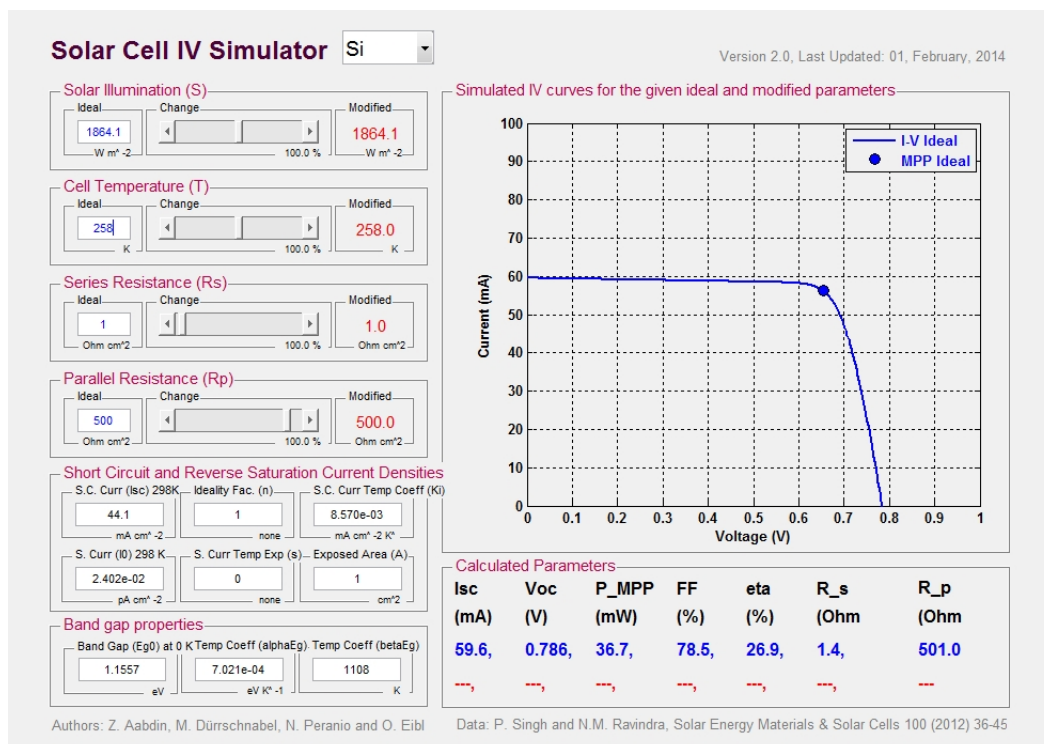


Figure 9: The simulation of the I-U curve for -15°C

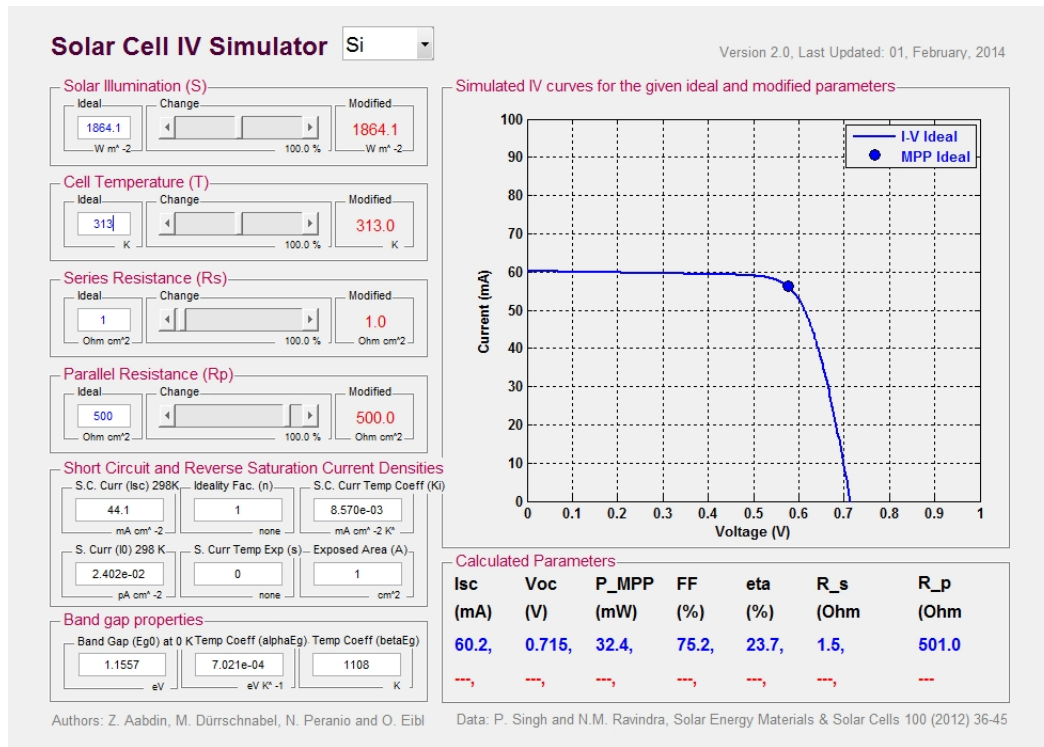


Figure 10: The simulation of the I-U curve for 40°C

temperature	I_{sc} (mA)	V_{oc} (V)	P_{MPP} (mW)	FF (%)	η (%)
-15°C	59.6	0.786	36.7	78.5	26.9
25°C	60	0.734	33.5	76.1	24.5
40°C	60.2	0.715	32.4	75.2	23.7

Table 4: results of the simulation with respect to the temperature

It can be assessed that the maximum power as well as the efficiency decrease with increasing temperature. This fact is in some extend of course counter productive to the practical application.

5 Conclusion

With the measurement results we can only partly be satisfied. The I-U curves and the P-U curves of the measured data showed a nice course, but especially for the I-U curves the measurement range was a little bit too small to get really good results for the parallel resistance. Despite that our results for the maximum Power and efficiency were good and valid. Because these are the most important values of the solar cell, we have been never the less capable to characterize our solar cell quite aptly. By also taking a look at the simulations for the effect of the temperature, we could further understand some of the difficulties that occur, when using solar cells in practice.